

Indian Institute of Technology Jodhpur, Year 2018

# Analog Electronics

(Course Code: EE314)

## Lecture 36-37: Feedback

**Course Instructor: Shree Prakash Tiwari**

Email: [sptiwari@iitj.ac.in](mailto:sptiwari@iitj.ac.in)


Webpage: <http://home.iitj.ac.in/~sptiwari/>

Course related documents will be uploaded on  
<http://home.iitj.ac.in/~sptiwari/EE314/>

**Note:** The information provided in the slides are taken from text books for microelectronics (including Sedra & Smith, B. Razavi), and various other resources from internet, for teaching/academic use only

1


## Negative Feedback System

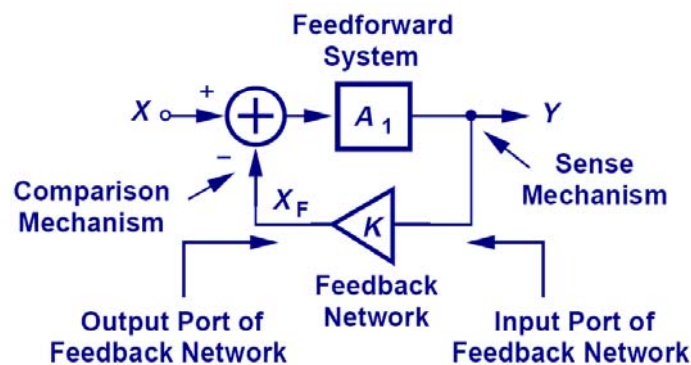

- A negative feedback system consists of four components: 1) feedforward system, 2) sense mechanism, 3) feedback network, and 4) comparison mechanism.

2


## Close-loop Transfer Function

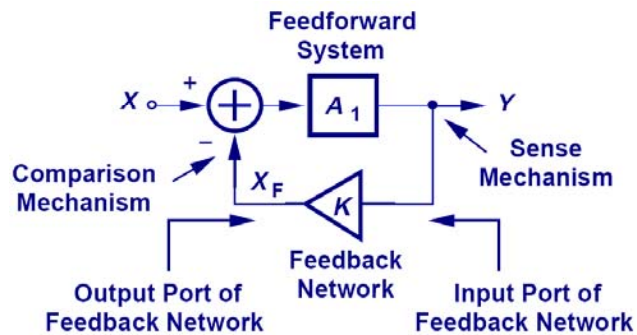

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$

3

## Feedback Example

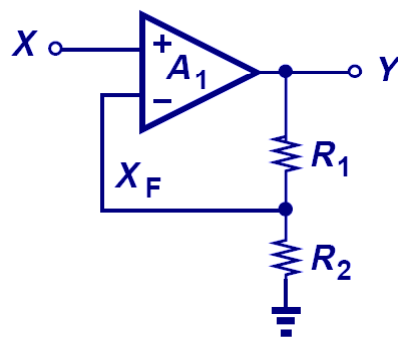


$$\frac{Y}{X} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1}$$

- $A_1$  is the feedforward network,  $R_1$  and  $R_2$  provide the sensing and feedback capabilities, and comparison is provided by differential input of  $A_1$ .

4

## Comparison Error

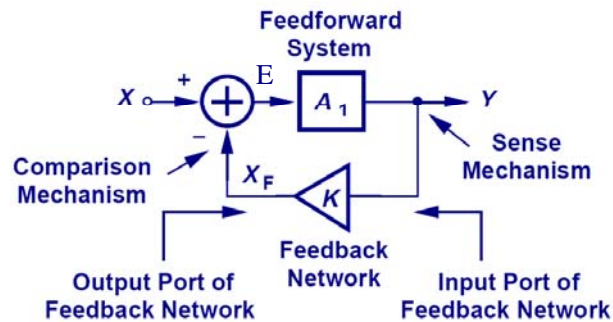


$$E = \frac{X}{1 + A_1 K}$$

- As  $A_1 K$  increases, the error between the input and feedback signal decreases. Or the feedback signal approaches a good replica of the input.

5


## Comparison Error

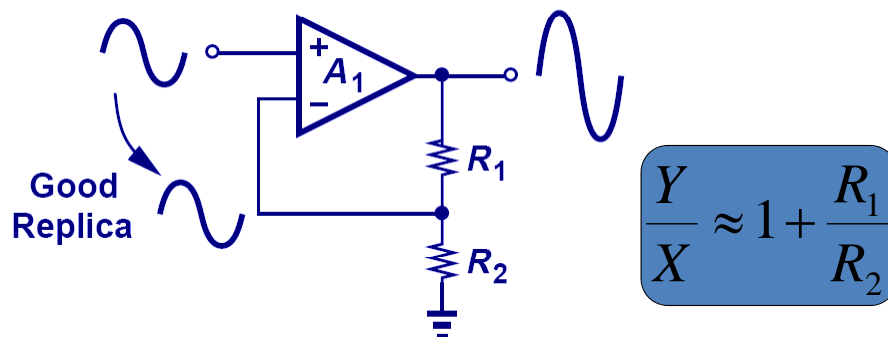

$$\frac{Y}{X} \approx 1 + \frac{R_1}{R_2}$$

6


## Loop Gain

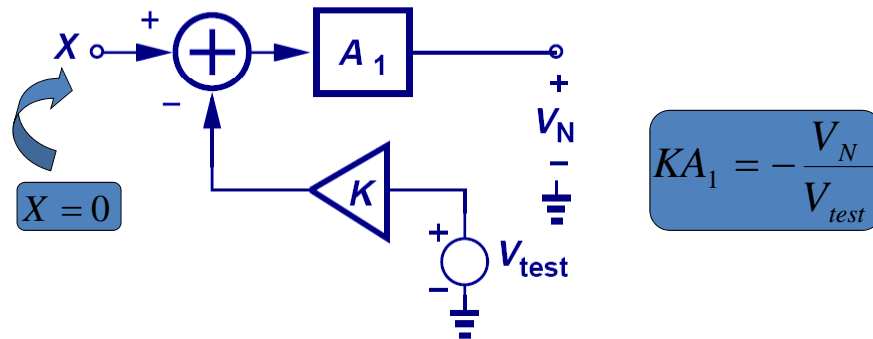

- When the input is grounded, and the loop is broken at an arbitrary location, the loop gain is measured to be  $KA_1$ .


7
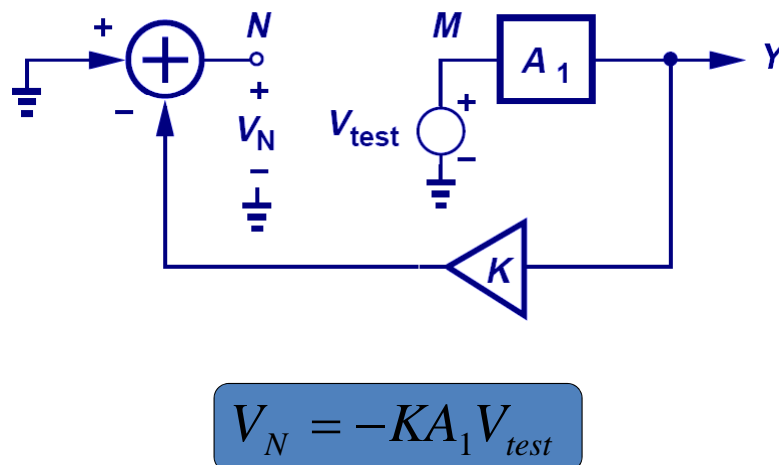
## Example: Alternative Loop Gain Measurement



8


## Incorrect Calculation of Loop Gain

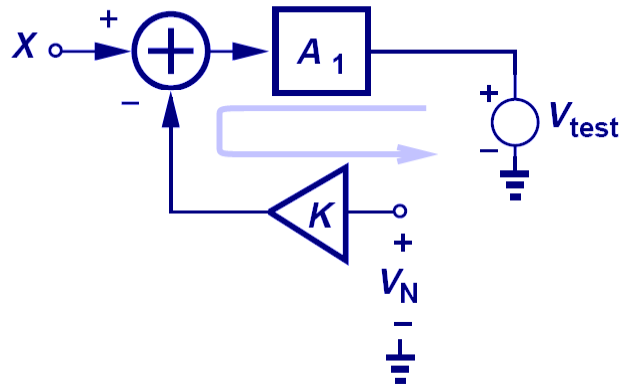

- Signal naturally flows from the input to the output of a feedforward/feedback system. If we apply the input the other way around, the “output” signal we get is not a result of the loop gain, but due to poor isolation.

9

## Gain Desensitization

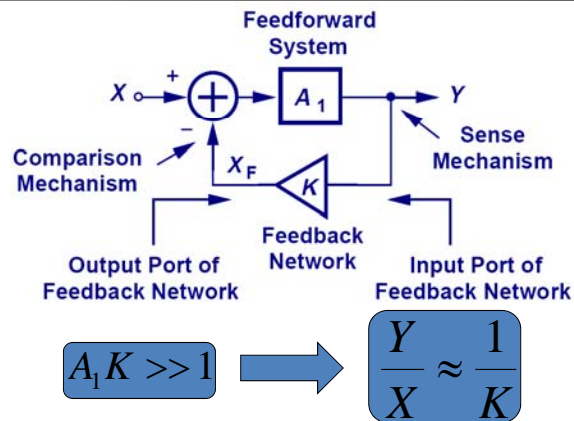


- A large loop gain is needed to create a precise gain, one that does not depend on  $A_1$ , which can vary by  $\pm 20\%$ .

10

## Ratio of Resistors

---

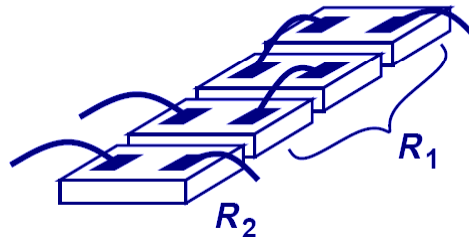

- When two resistors are composed of the same unit resistor, their ratio is very accurate. Since when they vary, they will vary together and maintain a constant ratio.

11


## Merits of Negative Feedback

---

- 1) Bandwidth enhancement
- 2) Modification of I/O Impedances
- 3) Linearization

12


## Bandwidth Enhancement

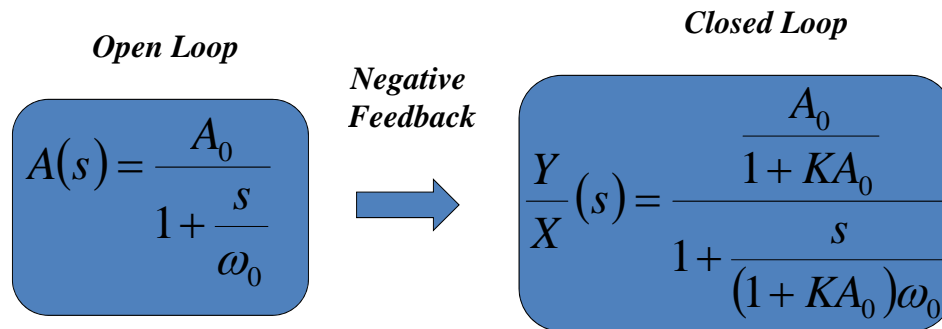

- Although negative feedback lowers the gain by  $(1+KA_0)$ , it also extends the bandwidth by the same amount.

13


## Bandwidth Extension Example

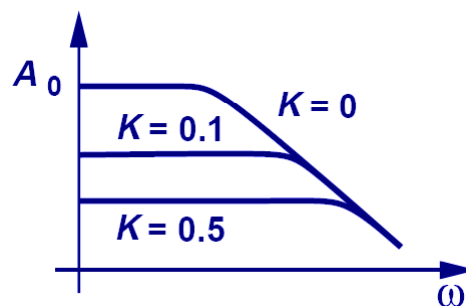

- As the loop gain increases, we can see the decrease of the overall gain and the extension of the bandwidth.

14


## Example: Open Loop Parameters

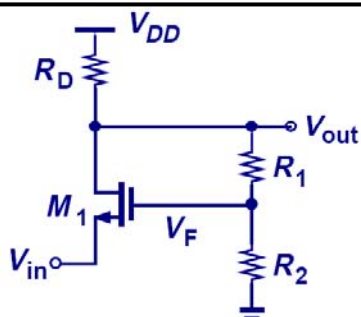

$$\begin{aligned} A_0 &\approx g_m R_D \\ R_{in} &= \frac{1}{g_m} \\ R_{out} &= R_D \end{aligned}$$

15

## Example: Closed Loop Voltage Gain

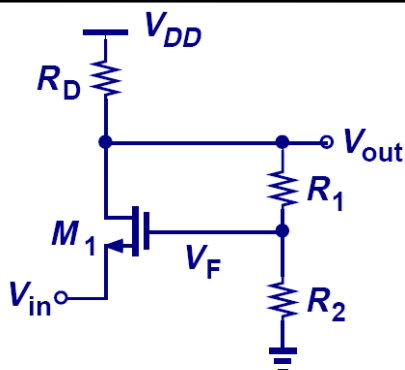


$$\frac{v_{out}}{v_{in}} = \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

16



## Example: Closed Loop I/O Impedance

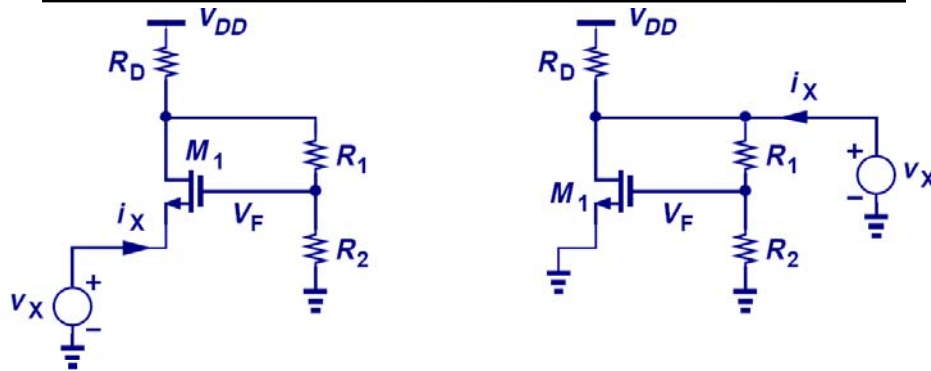


$$R_{in} = \frac{1}{g_m} \left( 1 + \frac{R_2}{R_1 + R_2} g_m R_D \right)$$

$$R_{out} = \frac{R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

17

## Example: Load Desensitization

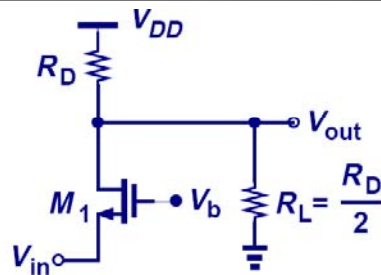

*W/O Feedback*  
*Large Difference*


$$g_m R_D \rightarrow g_m R_D / 3$$

*With Feedback*  
*Small Difference*

$$\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} \rightarrow \frac{g_m R_D}{3 + \frac{R_2}{R_1 + R_2} g_m R_D}$$


18

## Linearization

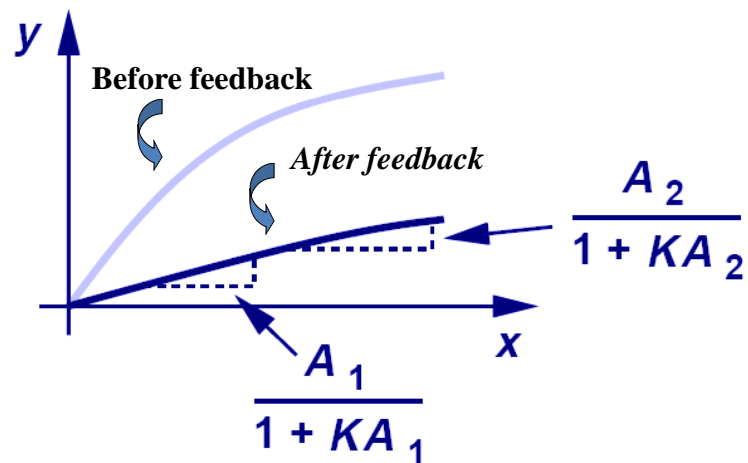

19


## Four Types of Amplifiers

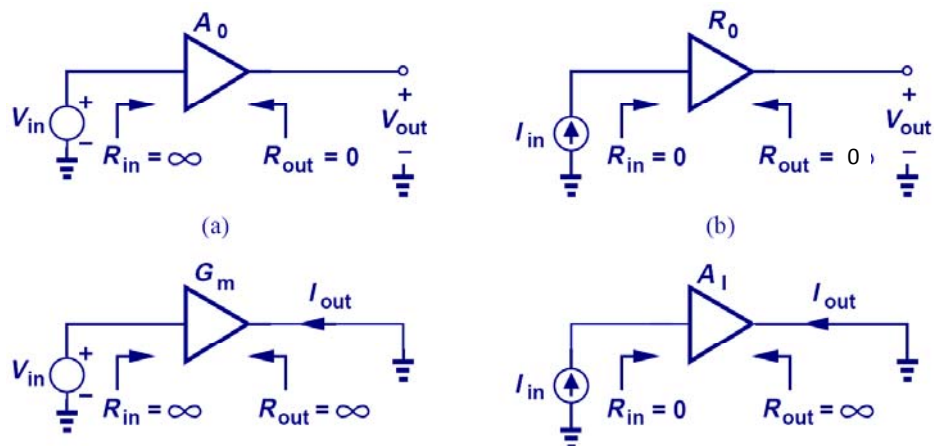

20

## Ideal Models of the Four Amplifier Types


---

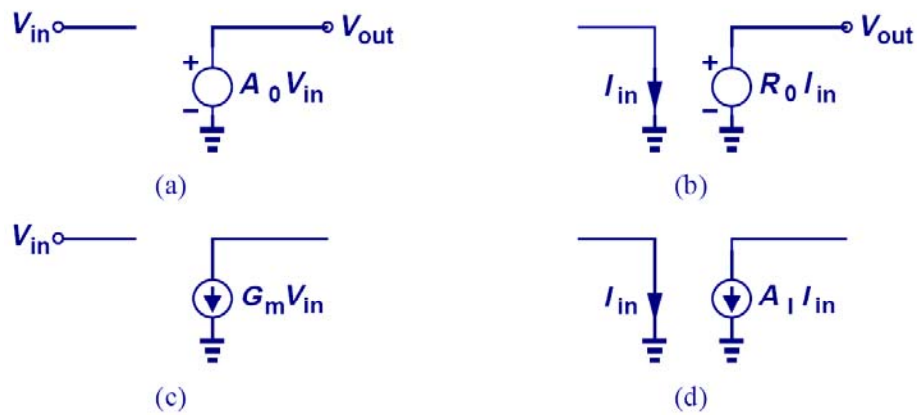

21


## Realistic Models of the Four Amplifier Types

---

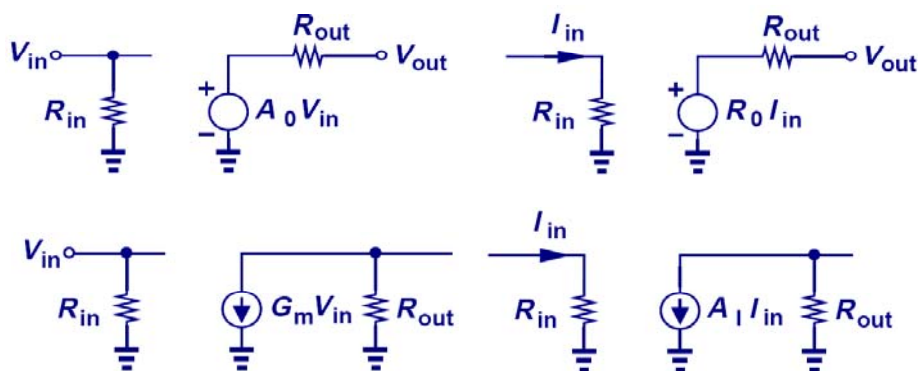


22

## Examples of the Four Amplifier Types

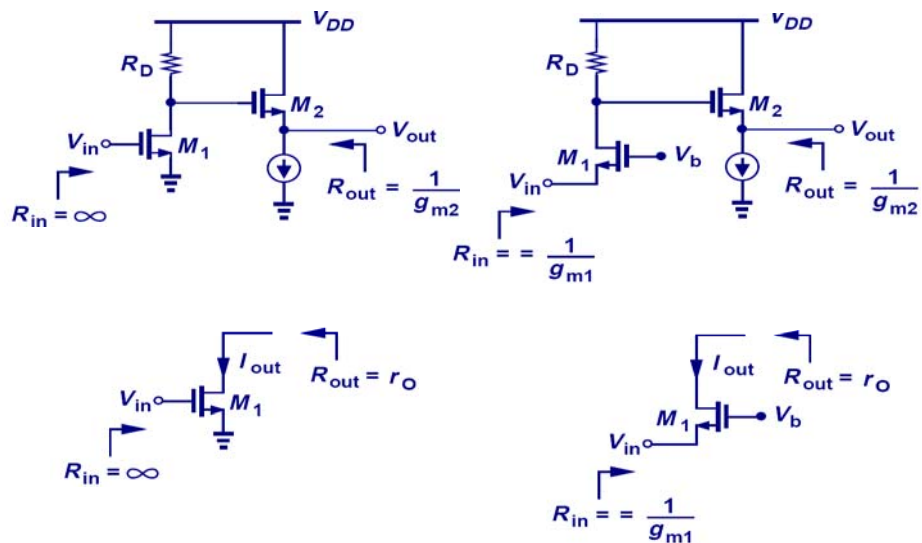


## Sensing a Voltage

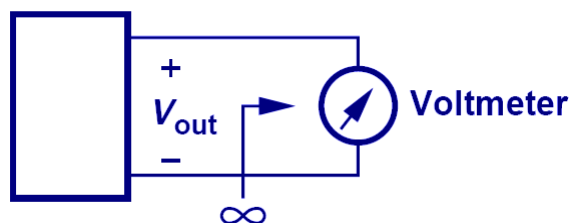

- In order to sense a voltage across two terminals, a voltmeter with ideally infinite impedance is used.


## Sensing and Returning a Voltage

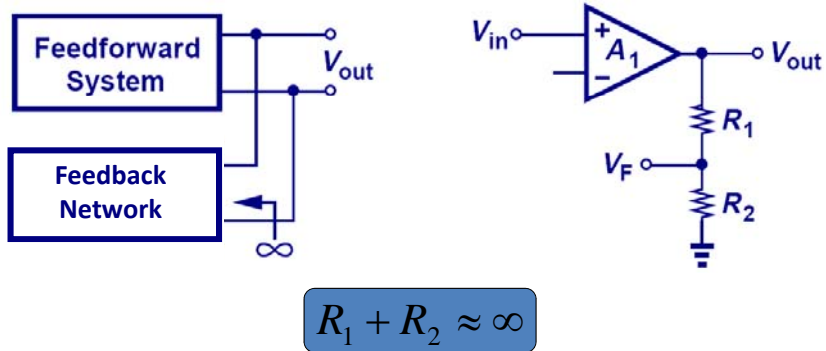

- Similarly, for a feedback network to correctly sense the output voltage, its input impedance needs to be large.
- $R_1$  and  $R_2$  also provide a mean to return the voltage.

25


## Sensing a Current

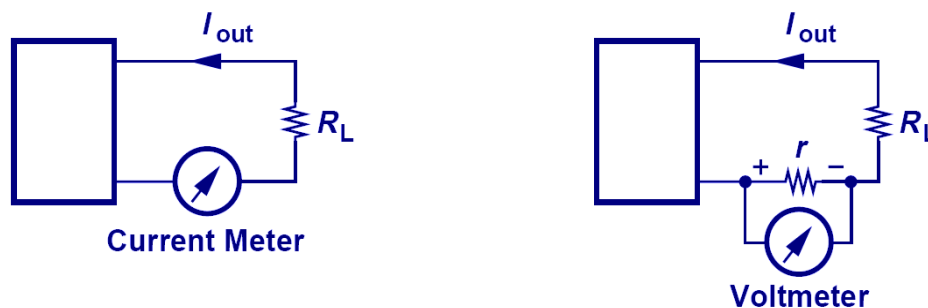

- A current is measured by inserting a current meter with ideally zero impedance in series with the conduction path.
- The current meter is composed of a small resistance  $r$  in parallel with a voltmeter.

26


## Sensing and Returning a Current

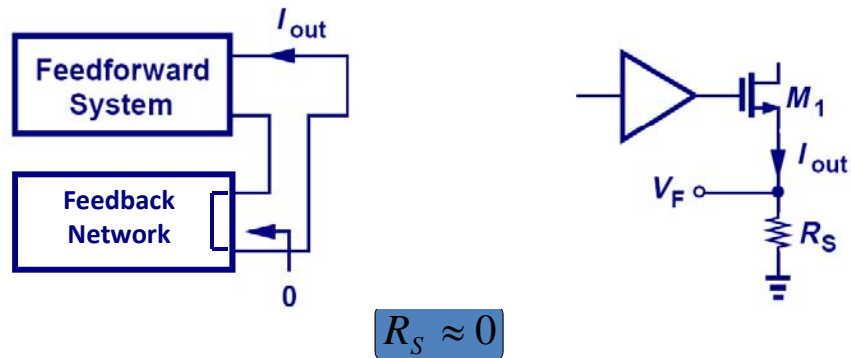

- Similarly for a feedback network to correctly sense the current, its input impedance has to be small.
- $R_S$  has to be small so that its voltage drop will not change  $I_{out}$ .

27



## Addition of Two Voltage Sources

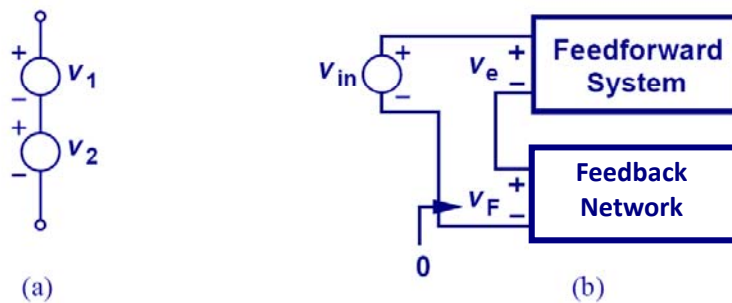

- In order to add or subtract two voltage sources, we place them in series. So the feedback network is placed in series with the input source.

28

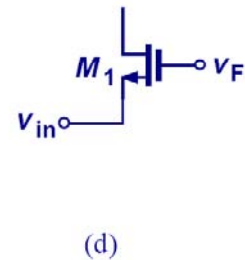
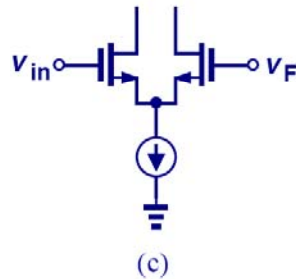
## Practical Circuits to Subtract Two Voltage Sources



- Although not directly in series,  $V_{in}$  and  $V_F$  are being subtracted since the resultant currents, differential and single-ended, are proportional to the difference of  $V_{in}$  and  $V_F$ .

29


## Addition of Two Current Sources

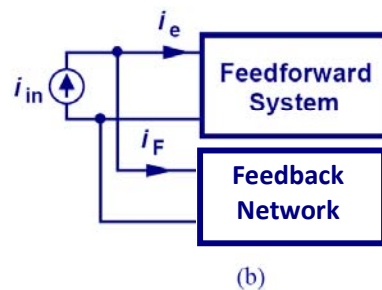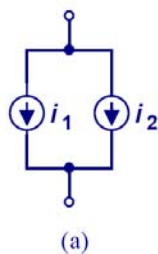

- In order to add two current sources, we place them in parallel. So the feedback network is placed in parallel with the input signal.

30

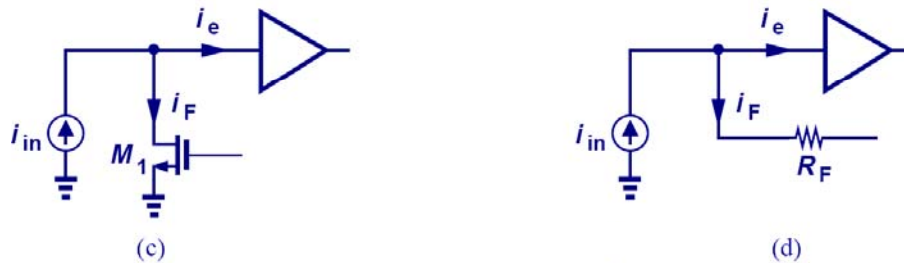
## Practical Circuits to Subtract Two Current Sources



- Since  $M_1$  and  $R_F$  are in parallel with the input current source, their respective currents are being subtracted. Note,  $R_F$  has to be large enough to approximate a current source.

31

## Example: Sense and Return

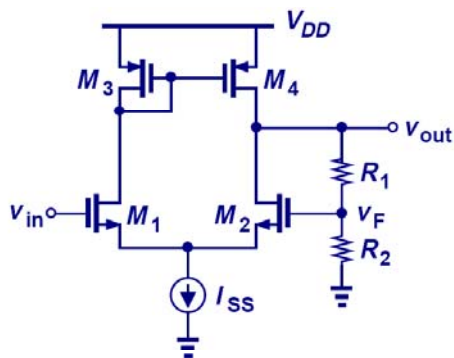


- $R_1$  and  $R_2$  sense and return the output voltage to feedforward network consisting of  $M_1$ -  $M_4$ .
- $M_1$  and  $M_2$  also act as a voltage subtractor.

32




## Example: Feedback Factor

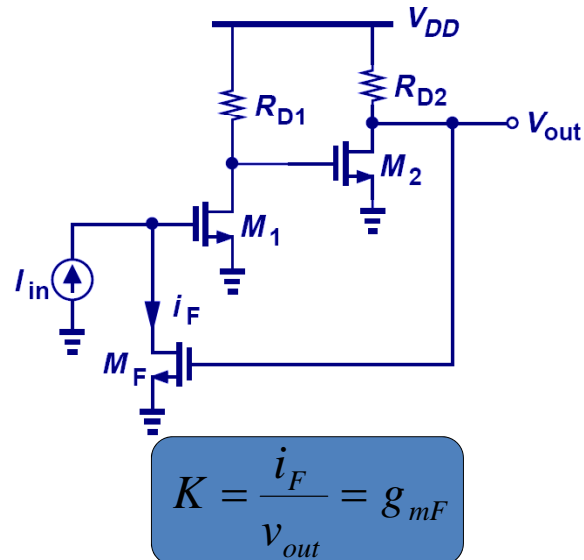

33

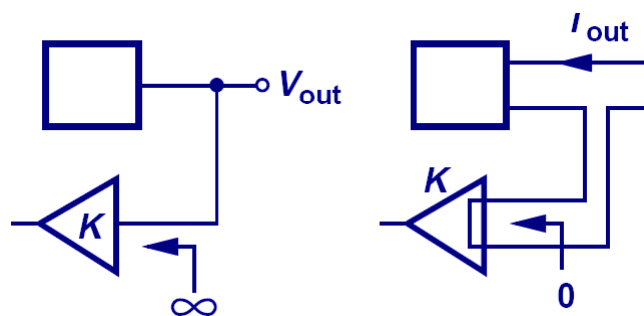
## Input Impedance of an Ideal Feedback Network



- To sense a voltage, the input impedance of an ideal feedback network must be infinite.
- To sense a current, the input impedance of an ideal feedback network must be zero.

34
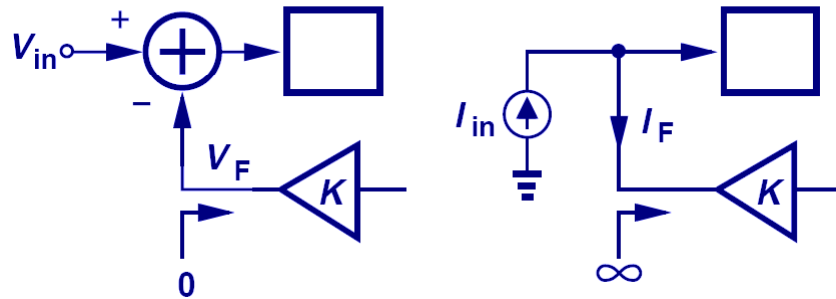
## Output Impedance of an Ideal Feedback Network



- To return a voltage, the output impedance of an ideal feedback network must be zero.
- To return a current, the output impedance of an ideal feedback network must be infinite.


35

## Determining the Polarity of Feedback

- 1) Assume the input goes either up or down.
- 2) Follow the signal through the loop.
- 3) Determine whether the returned quantity enhances or opposes the original change.

36

## Polarity of Feedback Example I

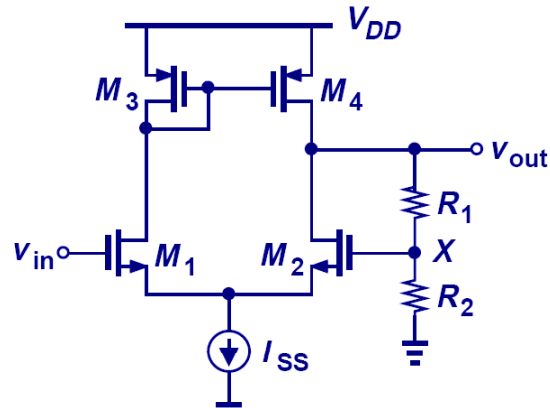


$V_{in} \uparrow \Rightarrow I_{D1} \uparrow, I_{D2} \downarrow \Rightarrow V_{out} \uparrow, V_x \uparrow \Rightarrow I_{D2} \uparrow, I_{D1} \downarrow$

*Negative Feedback*

37

## Polarity of Feedback Example II

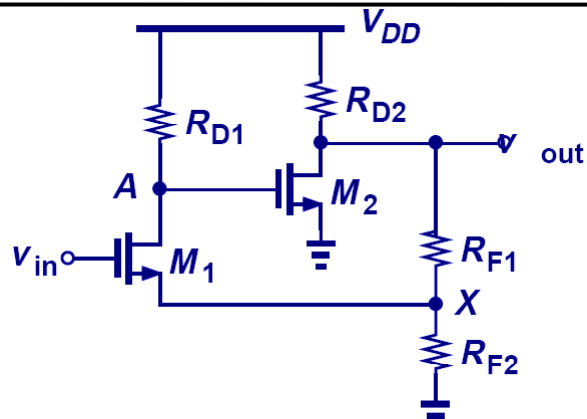


$V_{in} \uparrow \Rightarrow I_{D1} \uparrow, V_A \downarrow \Rightarrow V_{out} \uparrow, V_x \uparrow \Rightarrow I_{D1} \downarrow, V_A \uparrow$

*Negative Feedback*


38

## Polarity of Feedback Example III

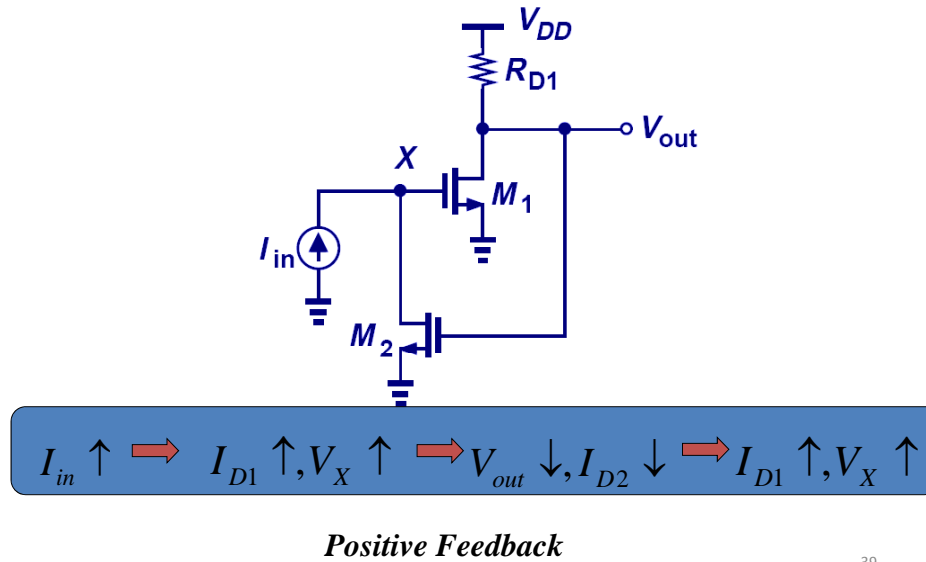

39


## Voltage-Voltage Feedback

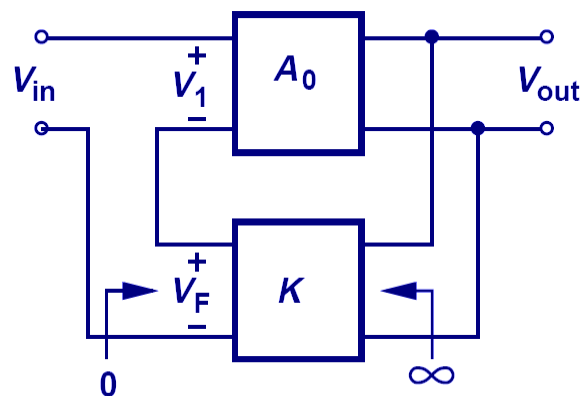

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + KA_0}$$

40


## Example: Voltage-Voltage Feedback

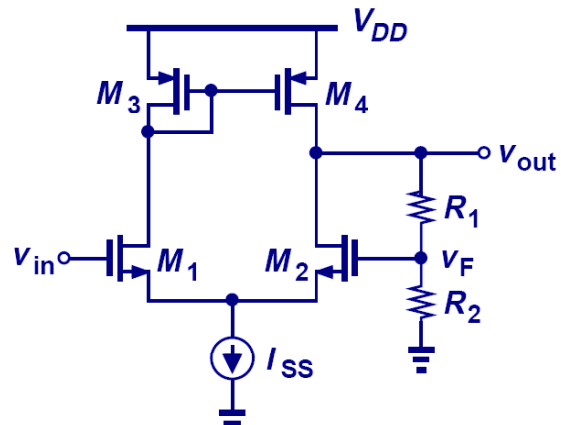

$$\frac{V_{out}}{V_{in}} = \frac{g_{mN} (r_{ON} \parallel r_{OP})}{1 + \frac{R_2}{R_1 + R_2} g_{mN} (r_{ON} \parallel r_{OP})}$$

41

## Input Impedance of a V-V Feedback

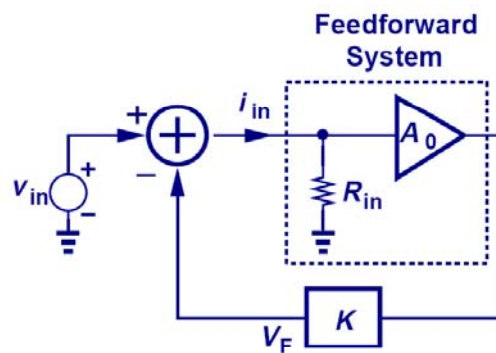


$$\frac{V_{in}}{I_{in}} = R_{in} (1 + A_0 K)$$

- A better voltage sensor

42

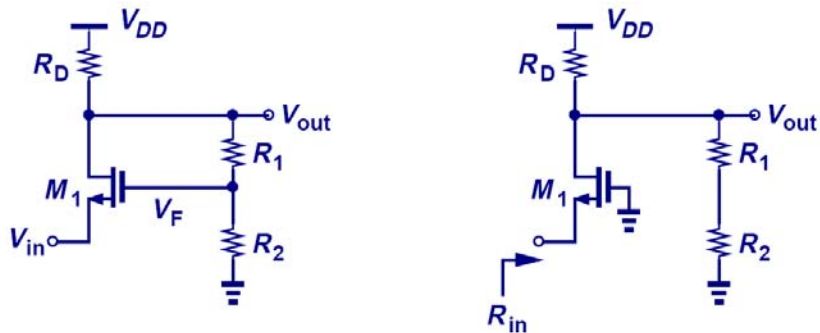
### Example: V-V Feedback Input Impedance



$$\frac{V_{in}}{I_{in}} = \frac{1}{g_m} \left( 1 + \frac{R_2}{R_1 + R_2} g_m R_D \right)$$

43


### Output Impedance of a V-V Feedback

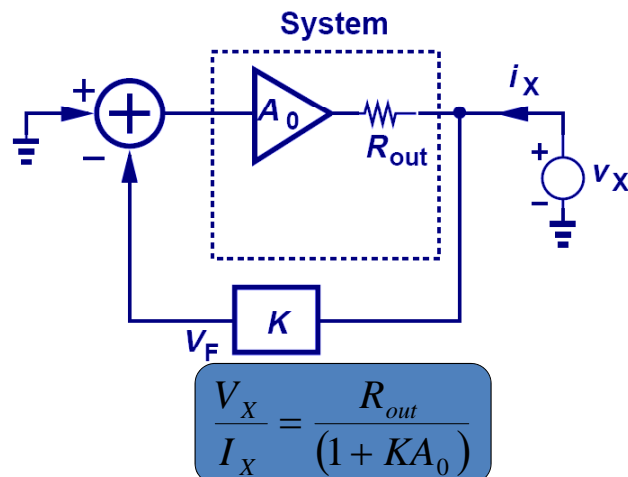

- A better voltage source

44

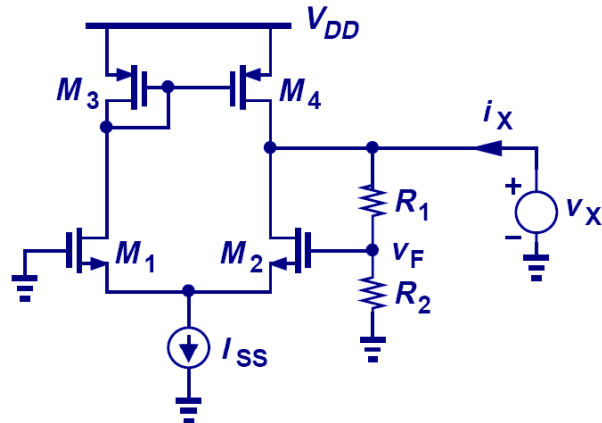
### Example: V-V Feedback Output Impedance



$$R_{out, closed} \approx \left(1 + \frac{R_1}{R_2}\right) \frac{1}{g_{mN}}$$

45


### Voltage-Current Feedback

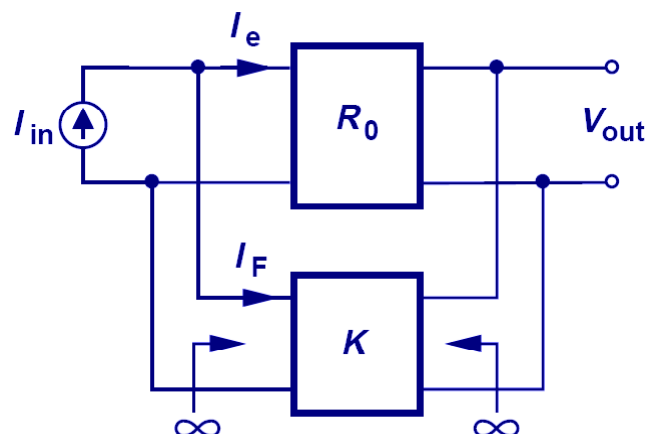

$$\frac{V_{out}}{I_{in}} = \frac{R_O}{1 + KR_O}$$


46

## Example: Voltage-Current Feedback

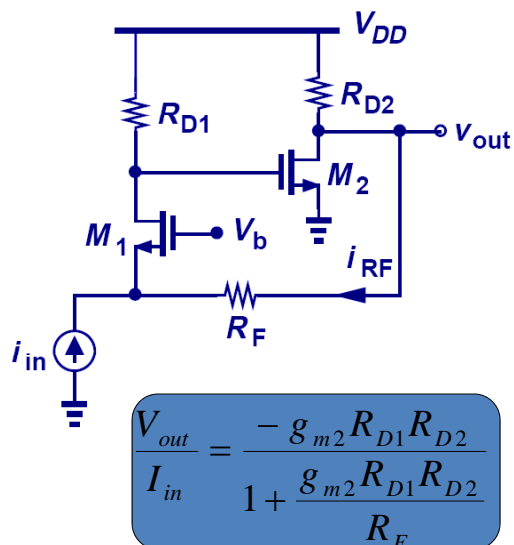

47

## Input Impedance of a V-C Feedback

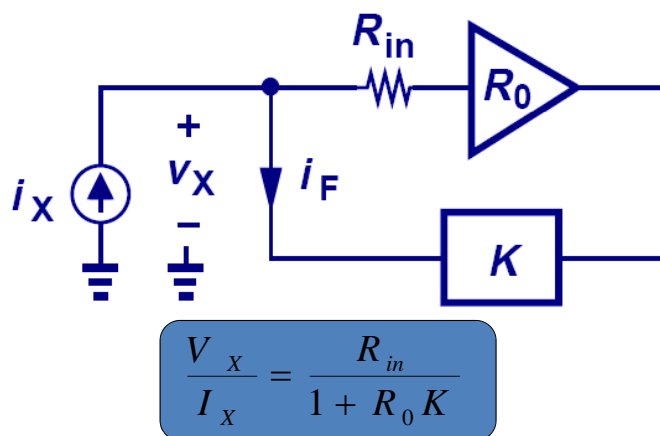


- A better current sensor.

48



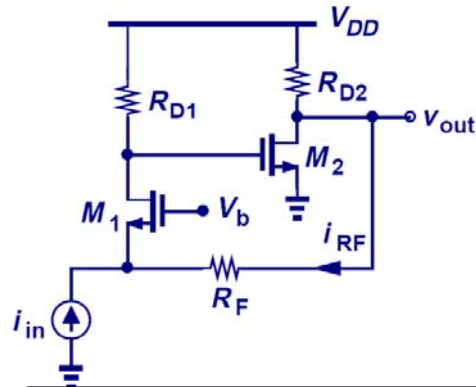
### Example: V-C Feedback Input Impedance



$$R_{in,closed} = \frac{1}{g_{m1}} \cdot \frac{1}{1 + \frac{g_{m2} R_{D1} R_{D2}}{R_F}}$$

49

### Output Impedance of a V-C Feedback

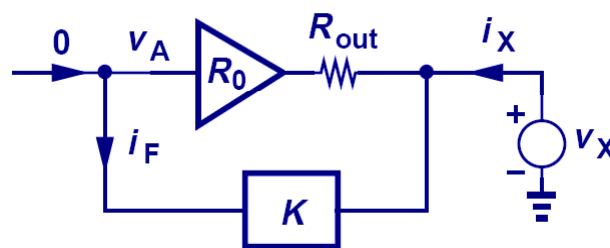


$$\frac{V_X}{I_X} = \frac{R_{out}}{1 + R_0 K}$$

- A better voltage source.

50
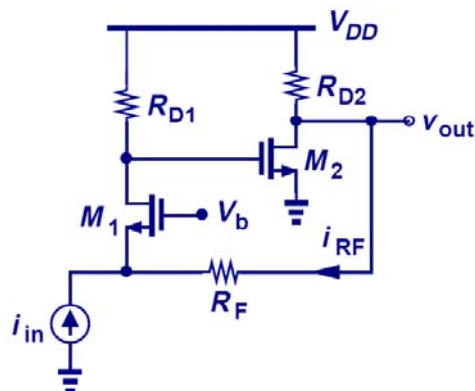
## Example: V-C Feedback Output Impedance



$$R_{out, closed} = \frac{R_{D2}}{1 + \frac{g_{m2} R_{D1} R_{D2}}{R_F}}$$

51

## What next

- Feedback contd..